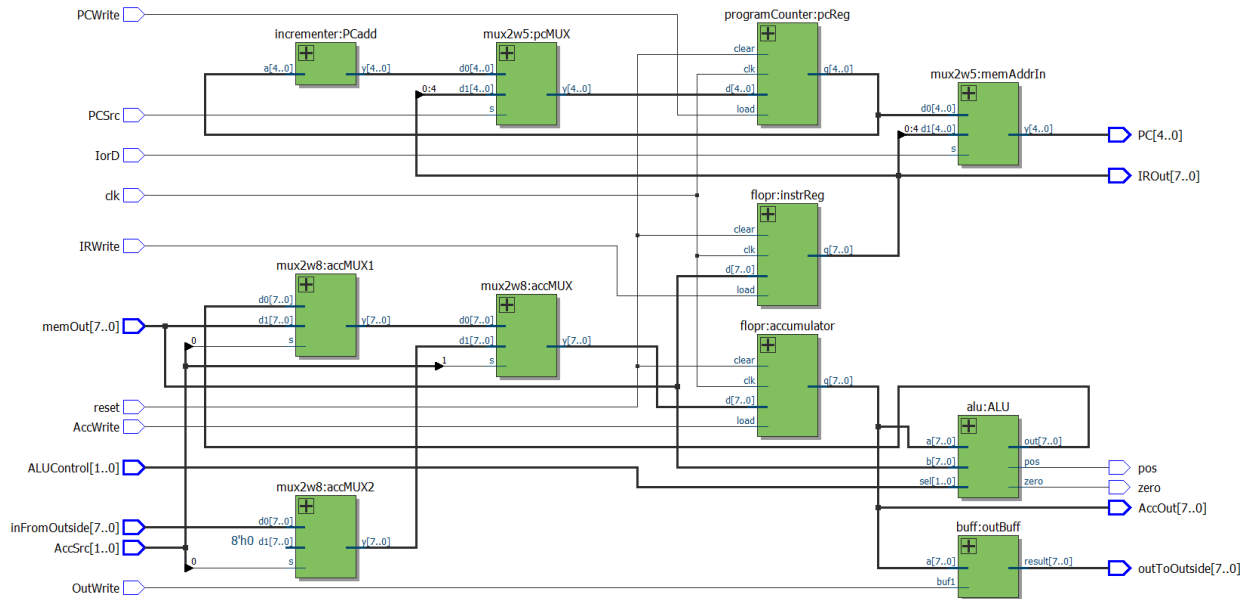



Final Report

1. Schematic of the DATAPATH (from RTL Viewer)




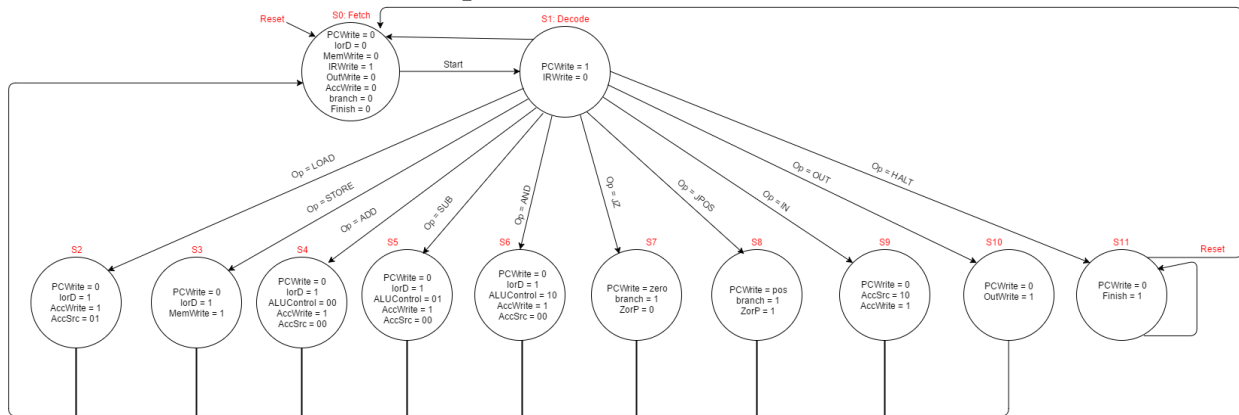2. Control Unit

State Graph of Finite State Machine (FSM)



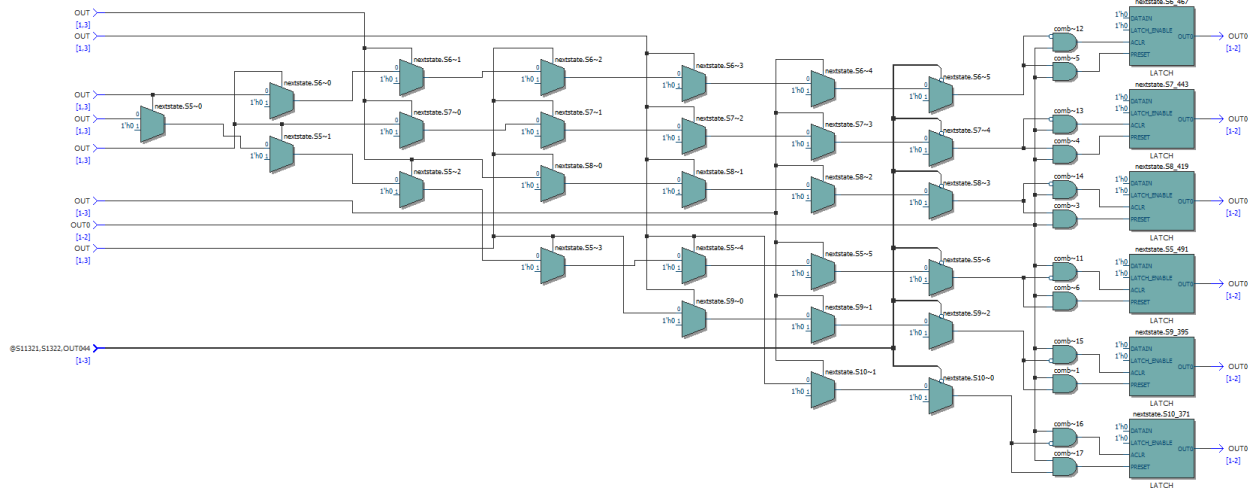Schematic of Control Unit (from RTL Viewer)



Control Word Table (Per Cycle Per Instruction)

Instr	St	ZorP	branch	PCWrite	IorD	MemWrite	IRWrite	OutWrite	AccSrc	AccWrite	ALUControl
LOAD	F	X	0	0	0	0	1	0	XX	0	XX
	D	X	0	1	0	0	0	0	XX	0	XX
	E	X	0	0	1	0	0	0	01	1	XX
STORE	F	X	0	0	0	0	1	0	XX	0	XX
	D	X	0	1	0	0	0	0	XX	0	XX
	E	X	0	0	1	1	0	0	XX	0	XX
ADD	F	X	0	0	0	0	1	0	XX	0	XX
	D	X	0	1	0	0	0	0	XX	0	XX
	E	X	0	0	1	0	0	0	00	1	00
SUB	F	X	0	0	0	0	1	0	XX	0	XX
	D	X	0	1	0	0	0	0	XX	0	XX
	E	X	0	0	1	0	0	0	00	1	01
AND	F	X	0	0	0	0	1	0	XX	0	XX
	D	X	0	1	0	0	0	0	XX	0	XX
	E	X	0	1	0	0	0	0	00	1	10
JZ	F	X	0	0	0	0	1	0	XX	0	XX
	D	X	0	1	0	0	0	0	XX	0	XX
	E	0	1	zero	0	0	0	0	XX	0	XX
JPOS	F	X	0	0	0	0	1	0	XX	0	XX
	D	X	0	1	0	0	0	0	XX	0	XX
	E	1	1	pos	0	0	0	0	XX	0	XX
IN	F	X	0	0	0	0	1	0	XX	0	XX
	D	X	0	1	0	0	0	0	XX	0	XX
	E	X	0	0	0	0	0	0	10	1	XX
OUT	F	X	0	0	0	0	1	0	XX	0	XX
	D	X	0	1	0	0	0	0	XX	0	XX
	E	X	0	0	0	0	0	1	XX	0	XX
HALT	F	X	0	0	0	0	1	0	XX	0	XX
	D	X	0	1	0	0	0	0	XX	0	XX
	E	X	0	0	0	0	0	0	XX	0	XX

3. Verilog Modules

Components of the Datapath

alu.v (Arithmetic Logic Unit)

```
/* Reiner Dizon
 * CPE 300 Take Home Final
 * Simple 8-bit microprocessor (MP-8)
 * Arithmetic Logic Unit (ALU) Module
 */
module alu (a, b, sel, out, zero, pos);
    input [7:0] a, b;          // a - Accumulator, b - Memory
    input [1:0] sel;           // from Control Unit (ALUControl signal)
    output reg [7:0] out;      // fed back to Accumulator MUX
    output reg zero, pos;      // used for JZ, JPOS instructions

    initial begin
        out = 0;
        zero = 1'b0;
        pos = 1'b0;
    end

    always @ (*) begin
        case(sel)
            2'b00: begin // ADD
                out = a + b;
                if(a == 0) zero = 1;
                else zero = 0;
                if(a > 0) pos = 1;
                else pos = 0;
            end
            2'b01: begin // SUB
                out = a - b;
                if(a == 0) zero = 1;
                else zero = 0;
                if(a > 0) pos = 1;
                else pos = 0;
            end
            2'b10: begin // AND
                out = a & b;
                if(a == 0) zero = 1;
                else zero = 0;
                if(a > 0) pos = 1;
                else pos = 0;
            end
        endcase
    end
endmodule
```

buff.v (Tri-State Buffer)

```
/* Reiner Dizon
 * CPE 300 Take Home Final
 * Simple 8-bit microprocessor (MP-8)
 * Tri-State Buffer Module
 */
module buff(
    output reg [7:0] result,      // Data Output
    input [7:0] a,                // Tri-State Bus Control
    input buf1                    // Data Input
);
    always @(*)
        if(buf1 == 1)
            result = a;
        else
            result = 8'bzzzz_zzzz;
endmodule
```

flopr.v (Resettable Register)

```
/* Reiner Dizon
 * CPE 300 Take Home Final
 * Simple 8-bit microprocessor (MP-8)
 * Resettable Flip-Flop Module
 * (Accumulator & Instruction Register)
 */
module flopr(
    input clk, clear, load,      // clock, clear, & load
    input [7:0] d,              // data in
    output reg [7:0] q          // data out
);
    // used for Accumulator & Instruction Register
    always @(posedge clk, posedge clear)
        if(clear) q <= 0;
        else if(load) q <= d;
endmodule
```

incrementer.v (Incrementer)

```
/* Reiner Dizon
 * CPE 300 Take Home Final
 * Simple 8-bit microprocessor (MP-8)
 * Incrementer Module
 */
module incrementer (input [4:0] a, output [4:0] y);
    assign y = a + 1; // takes 5-bit input and adds 1, used for PC
endmodule
```

mux2w5.v (2-to-1 MUX with 5-bit Data Width)

```
/* Reiner Dizon
 * CPE 300 Take Home Final
 * Simple 8-bit microprocessor (MP-8)
 * 2-to-1 MUX with 5-bit Data Width Module
 */
module mux2w5(
    input [4:0] d0, d1,      // Two Data Inputs
    input s,                // Selector Input (from Control Unit)
    output [4:0] y           // MUX Output
);
    assign y = s ? d1 : d0;
endmodule
```

mux2w8.v (2-to-1 MUX with 8-bit Data Width)

```
/* Reiner Dizon
 * CPE 300 Take Home Final
 * Simple 8-bit microprocessor (MP-8)
 * 2-to-1 MUX (8-bit data width) Module
 */
module mux2w8(
    input [7:0] d0, d1,      // Two Data Inputs
    input s,                // Selector Input (from Control Unit)
    output [7:0] y           // MUX Output
);
    assign y = s ? d1 : d0;
endmodule
```

programCounter.v (Program Counter Register)

```
/* Reiner Dizon
 * CPE 300 Take Home Final
 * Simple 8-bit microprocessor (MP-8)
 * Program Counter Register Module
 */
module programCounter(
    input clk, clear, load,  // Clock, Clear, & Load Signal
    input [4:0] d,           // Data Input
    output reg [4:0] q       // Data Output
);
    always @(posedge clk, posedge clear)
        if(clear) q <= 0;
        else if(load) q <= d;
endmodule
```

Datapath – datapath.v

```
/* Reiner Dizon
 * CPE 300 Take Home Final
 * Simple 8-bit microprocessor (MP-8)
 * Datapath Module
 */
module datapath(
    input clk, reset,                // Clock & Reset Input
    input PCWrite, IorD, PCSrc,      // *
    input IRWrite, AccWrite, OutWrite, // * Signals from Control Unit
    input [1:0] AccSrc, ALUControl,  // *
    output zero, pos,                // Branch Condition Signals: used
    for JZ, JPOS instructions
    output [4:0] PC,                  // Program Counter Output
    input [7:0] memOut, inFromOutside, // Output From Memory & Outside:
    comes from Top Module
    output [7:0] IROut,               // Instruction Register Output
    output [7:0] AccOut, outToOutside // Accumulator Output & Output to
    Outside: used for Top Module
);
    wire [4:0] pcRegIn, pcRegOut, PCplus1;
    wire [7:0] accMUX1out, accMUX2out, accIn;
    wire [7:0] ALUOut;

    // next PC logic
    mux2w5 pcMUX(PCplus1, IROut[4:0], PCSrc, pcRegIn);
    programCounter pcReg(clk, reset, PCWrite, pcRegIn, pcRegOut);
    incrementer PCadd(pcRegOut, PCplus1);
    mux2w5 memAddrIn(pcRegOut, IROut[4:0], IorD, PC);

    // instruction register
    flopr instrReg(clk, reset, IRWrite, memOut, IROut);

    // accumulator register
    mux2w8 accMUX1(ALUOut, memOut, AccSrc[0], accMUX1out);
    mux2w8 accMUX2(inFromOutside, 8'b0, AccSrc[0], accMUX2out);
    mux2w8 accMUX(accMUX1out, accMUX2out, AccSrc[1], accIn);
    flopr accumulator(clk, reset, AccWrite, accIn, AccOut);

    // ALU logic
    alu ALU(AccOut, memOut, ALUControl, ALUOut, zero, pos);

    // out tri-state buffer
    buff outBuff(outToOutside, AccOut, OutWrite);
endmodule
```

Controller/Control Unit – controller.v

```
/* Reiner Dizon
 * CPE 300 Take Home Final
 * Simple 8-bit microprocessor (MP-8)
 * Controller Module
 */
module controller(
    input clk, reset, start,          // Clock, Reset, & Start Signal
    input [7:0] instr,                // Instruction Input
    output PCSrc,
    output reg PCWrite, IorD, MemWrite,
    output reg IRWrite, OutWrite,
    output reg [1:0] AccSrc, ALUControl,
    output reg AccWrite,
    input zero, pos                    // Branch Condition Input (from ALU)
);
    reg branch, ZorP;
    reg [4:0] state;
    reg [4:0] nextstate;
    parameter S0 = 0; // reset
    parameter S1 = 1;
    parameter S2 = 2;
    parameter S3 = 3;
    parameter S4 = 4;
    parameter S5 = 5;
    parameter S6 = 6;
    parameter S7 = 7;
    parameter S8 = 8;
    parameter S9 = 9;
    parameter S10 = 10;
    parameter S11 = 11;

    always @(posedge clk, posedge reset)
        if(reset) state <= S0;
        else state <= nextstate;

    always @(state, instr, start) begin
        case(state)
            S0: begin
                if(start) begin
                    PCWrite <= 1'b0;
                    IorD <= 1'b0;
                    MemWrite <= 1'b0;
                    IRWrite <= 1'b1;
                    OutWrite <= 1'b0;
                    AccSrc <= 2'bxx;
                    AccWrite <= 1'b0;
                    ALUControl <= 2'bxx;
                    branch <= 1'b0;
                    ZorP <= 1'bx;
                    nextstate <= S1;
                end
                else nextstate <= S0;
            end
            S1: begin
```

```

        PCWrite <= 1'b1;
        IRWrite <= 1'b0;
        if(instr[7:5] == 3'b000) nextstate <= S2; //opcode = LOAD
        if(instr[7:5] == 3'b001) nextstate <= S3; //opcode = STORE
        if(instr[7:5] == 3'b010) nextstate <= S4; //opcode = ADD
        if(instr[7:5] == 3'b011) nextstate <= S5; //opcode = SUB
        if(instr[7:5] == 3'b100) nextstate <= S6; //opcode = AND
        if(instr[7:5] == 3'b101) nextstate <= S7; //opcode = JZ
        if(instr[7:5] == 3'b110) nextstate <= S8; //opcode = JPOS
        if(instr[7:3] == 5'b11100) nextstate <= S9; //opcode = IN
        if(instr[7:3] == 5'b11101) nextstate <= S10; //opcode = OUT
        if(instr[7:4] == 4'b1111) nextstate <= S11; //opcode = HALT
    end

S2: begin // LOAD
        PCWrite <= 1'b0;
        IorD <= 1'b1;
        AccWrite <= 1'b1;
        AccSrc <= 2'b01;
        nextstate <= S0;
    end

S3: begin // STORE
        PCWrite <= 1'b0;
        IorD <= 1'b1;
        MemWrite <= 1'b1;
        nextstate <= S0;
    end

S4: begin // ADD
        PCWrite <= 1'b0;
        IorD <= 1'b1;
        ALUControl <= 2'b00;
        AccSrc <= 2'b00;
        AccWrite <= 1'b1;
        nextstate <= S0;
    end

S5: begin // SUB
        PCWrite <= 1'b0;
        IorD <= 1'b1;
        ALUControl <= 2'b01;
        AccSrc <= 2'b00;
        AccWrite <= 1'b1;
        nextstate <= S0;
    end

S6: begin // AND
        PCWrite <= 1'b0;
        IorD <= 1'b1;
        ALUControl <= 2'b10;
        AccSrc <= 2'b00;
        AccWrite <= 1'b1;
        nextstate <= S0;
    end

```



```

S7: begin // JZ
    PCWrite <= zero;
    branch <= 1'b1;
    ZorP <= 1'b0;
    nextstate <= S0;
end

S8: begin // JPOS
    PCWrite <= pos;
    branch <= 1'b1;
    ZorP <= 1'b1;
    nextstate <= S0;
end

S9: begin // IN
    PCWrite <= 1'b0;
    AccSrc <= 2'b10;
    AccWrite <= 1'b1;
    nextstate <= S0;
end

S10: begin // OUT
    PCWrite <= 1'b0;
    OutWrite <= 1'b1;
    nextstate <= S0;
end

S11: begin // HALT
    PCWrite <= 1'b0;
    nextstate <= S11;
end
default: nextstate <= S0;
endcase
end
assign PCSrc = ZorP ? (branch & pos) : (branch & zero);
endmodule

```

Microprocessor – microProc.v

```

/* Reiner Dizon
 * CPE 300 Take Home Final
 * Simple 8-bit microprocessor (MP-8)
 * Microprocessor Module
 */
module microProc(
    input clk, reset, start,           // Clock, Reset, & Start Signal
    output [4:0] PC,                   // Program Counter Output
    input [7:0] inFromOutside, memOut, // Input From Outside, Memory
    Output
    output OutWrite, MemWrite,
    output [7:0] AccOut, outToOutside
);
    wire PCWrite, IorD, PCSrc, IRWrite, AccWrite;
    wire [1:0] ALUControl, AccSrc;
    wire zero, pos;
    wire [7:0] IROut;

```

```

    controller CU(
        clk, reset, start, IROut, PCSrc, PCWrite,
        IorD, MemWrite, IRWrite, OutWrite, AccSrc,
        ALUControl, AccWrite, zero, pos
    );
    datapath DP(
        clk, reset, PCWrite, IorD, PCSrc,
        IRWrite, AccWrite, OutWrite,
        AccSrc, ALUControl, zero, pos, PC,
        memOut, inFromOutside, IROut,
        AccOut, outToOutside
    );
endmodule

```

Combined Instruction/Data Memory – mem.v

```

/* Reiner Dizon
 * CPE 300 Take Home Final
 * Simple 8-bit microprocessor (MP-8)
 * Combined Instruction/Data Memory Module
 */
module mem(
    input CLK,                // Clock Input
    input [4:0] addr,         // Address Input (from MUX)
    input [7:0] WD,           // Write Data Input
    input WE,                 // Write Enable Input
    output [7:0] RD           // Read Data Output
);
    reg [7:0] RAM[31:0]; // RAM limited to 32-bit
    initial $readmemb("memfile.dat", RAM);
    assign RD = RAM[addr];
    always @(posedge CLK)
        if(WE) RAM[addr] <= WD;
endmodule

```

Top Module – top.v

```

/* Reiner Dizon
 * CPE 300 Take Home Final
 * Simple 8-bit microprocessor (MP-8)
 * Top Module
 */
module top(
    input clk, reset, start,                // Clock, Reset, &
    Start Input
    input [7:0] inFromOutside,               // Input from Outside
    output [7:0] AccOut, outToOutside, memOut, // Accumulator Output,
    Output from Outside, & Memory Output
    output [4:0] PC,                         // Program
    Counter/Address to the Memory
    output MemWrite, OutWrite                // Memory Write &
    OutWrite Signal (from Control Unit)
);
    microProc mp(
        clk, reset, start, PC, inFromOutside, memOut,
        OutWrite, MemWrite, AccOut, outToOutside
    );
    mem memory(clk, PC, AccOut, MemWrite, memOut);
endmodule

```

Testbench Module (For N = 5) – testb.v

```
/* Reiner Dizon
 * CPE 300 Take Home Final
 * Simple 8-bit microprocessor (MP-8)
 * Testbench Module
 */
module testb;
    reg clk, reset, start;
    reg [7:0] inFromOutside;
    wire [7:0] AccOut, outToOutside, memOut;
    wire [4:0] addr;
    wire MemWrite, OutWrite;

    // device under test
    top dut(clk, reset, start, inFromOutside, AccOut, outToOutside, memOut,
    addr, MemWrite, OutWrite);


    initial begin
        start <= 0;
        reset <= 1;
        #22;
        start <= 1;
        #22;
        reset <= 0;
        inFromOutside <= 5;
    end

    always begin
        clk <= 0;
        #5;
        clk <= 1;
        #5;
    end

    always @(posedge clk) begin
        if(addr == 30 && memOut == 15) begin
            $display ("Write Data:          Expected: 15
Actual: %d", memOut);
            $display ("Simulation succeeded");
        end
        else if(addr == 16) begin
            if(AccOut != 15) begin
                $display ("Write Data:          Expected: 15
Actual: %d", AccOut);
                $display ("Simulation failed");
            end
            $display ("Simulation done");
            $stop;
        end
    end
endmodule
```

[illegible]


For N = 5:
Waveform

 

Transcript

```
Transcript
VSIM 3> run -all
# Write Data:      Expected: 15      Actual:  15
# Simulation succeeded
# Simulation done
# ** Note: $stop   : C:/Users/Reiner/Desktop/CPE 300 Final/final/testb.v(44)
#   Time: 1445 ps  Iteration: 1  Instance: /testb
# Break in Module testb at C:/Users/Reiner/Desktop/CPE 300 Final/final/testb.v line 44
```

For N = 7:
Waveform

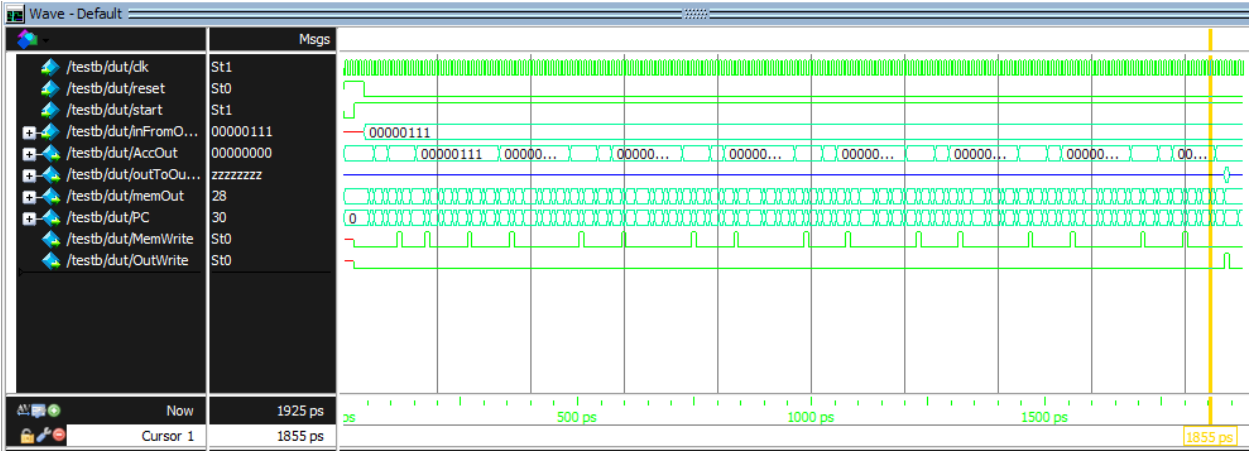

Transcript

```
Transcript
VSIM 7> run -all
# Write Data:      Expected: 28      Actual:  28
# Simulation succeeded
# Simulation done
# ** Note: $stop   : C:/Users/Reiner/Desktop/CPE 300 Final/final/testb.v(44)
#   Time: 1925 ps  Iteration: 1  Instance: /testb
# Break in Module testb at C:/Users/Reiner/Desktop/CPE 300 Final/final/testb.v line 44
```